

Name: \_\_\_\_\_  
Group: \_\_\_\_\_  
ID No : \_\_\_\_\_



**Future Technologies Industry Cluster**  
**College of VE, RMIT University**  
**AD026**  
**Electrical Principles EEET 2276**

**Tutorial # 02c**

**Kerchhoff's Voltage and Current Laws**  
**Voltage division in series circuits**

1. For the diagram shown bellow, state the value of the current  $I$  which flows in the circuit if the  $V_{AB}$  equals to 12 V. (show all calculation)

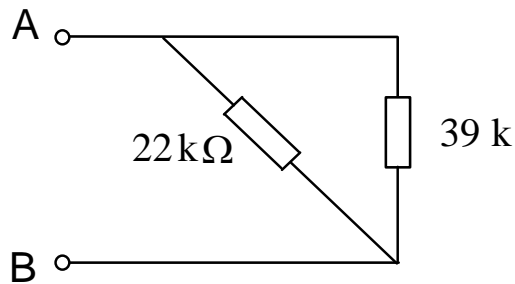


Fig 1

Calculation

2. a. For the circuit shown in Fig 2:

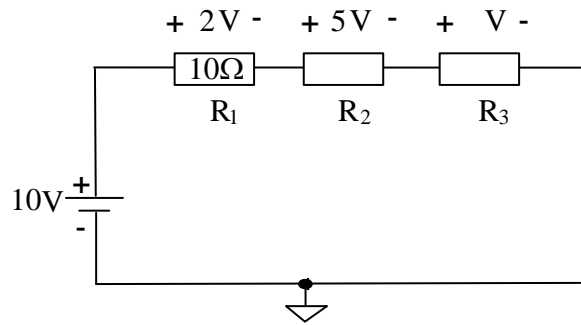


Fig 2

- (i) Determine the unknown voltage.

- (ii) Determine the values of the unknown resistors ( $R_2$  and  $R_3$ ).

- b. For the circuit shown in Fig 3:

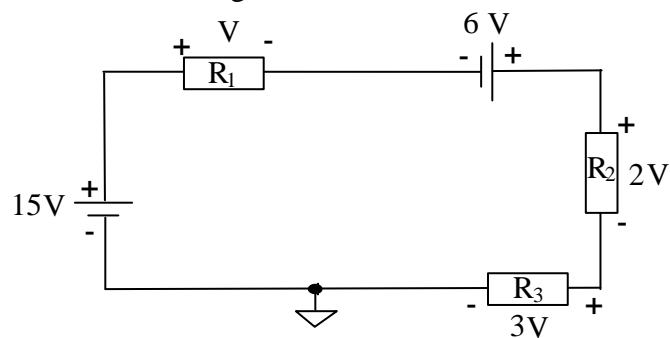


Fig 3

Determine the unknown voltage.

3. a. For the circuit shown in Fig 4:

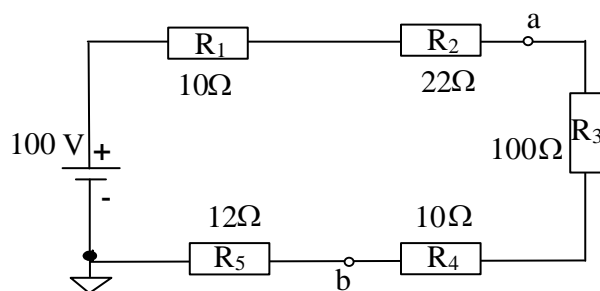


Fig 4

using the voltage divider rule, determine the voltage between a and b.

- b. For the circuit shown in Fig 5:

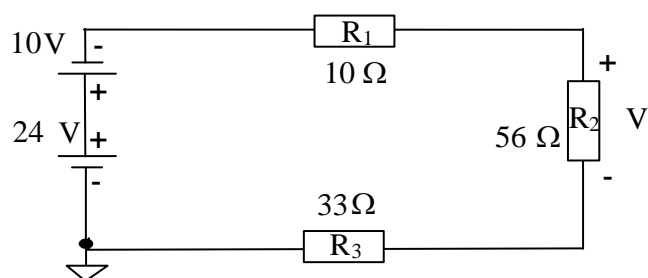


Fig 5

using the voltage divider rule, determine the voltage V.