

Name: \_\_\_\_\_

Group: \_\_\_\_\_



**Future Technologies Industry Cluster**  
**College of VE, RMIT University**  
**AD026**  
**Electrical Principles EEET 2276**

**Tutorial # 2a**

**Topics included in this tutorial are covered in the lectures of weeks 1 & 2 as shown below:**

- 1. Electrical fundamental quantities**
- 2. Resistors and color code**
- 3. Ohm's Law**
- 4. Series circuits**
- 5. Parrallel circuits**
- 6. Series – Parallel circuits**

1. The energy expended in moving a charge of 30 coulomb through a potential difference of 0.6 volts is:

- (a) 0.50 joules
- (b) 10 joules
- (c) 18 joules
- (d) 12 joules

2. If 0.18 coulomb of charge passes by a point every 7.5 ms then the current in amperes is equal to:

- (a) 24 Amps
- (b) 15 Amps
- (c) 1 Amps
- (d) 0 Amps

3. Cutting the area of a conductor in half

- (a) cuts the resistance in half
- (b) doubles the resistance
- (c) increases resistance 4 times
- (d) decreases resistance 4 times

4. A  $560\ \Omega$  with  $\pm 5\%$  tolerance resistor has the following colour code:

- (a) green, blue, red, red
- (b) green, blue, black, brown
- (c) green, blue, brown, silver
- (d) green, blue, brown, gold

5. A  $20\ \text{k}\Omega$  resistor has a conductance of:

- (a)  $7 \times 10^{-3}$
- (b)  $6 \times 10^6$
- (c)  $5 \times 10^{-5}$
- (d)  $4 \times 10^5$

6. Four  $220\ \Omega$ ,  $\pm 5\%$  resistors are measured with an ohmmeter. One of the measured resistor values is not within the  $\pm 5\%$  tolerance. Which one of the following readings is out of bounds?

7. A resistor has colour bands brown, black, silver and gold. The value of this resistor equals to:

- (a)  $0.1\ \Omega \pm 10\%$
- (b)  $1\ \Omega \pm 20\%$
- (c)  $100\ \Omega \pm 1\%$
- (d)  $0.1\ \Omega \pm 5\%$

8. A clock has an internal resistance of  $8.2\ \text{k}\Omega$ . The current through the clock if it is powered by a  $220\ \text{V}$  outlet equals to:

- (a)  $1\ \text{mAmp}$
- (b)  $26.83\ \text{mAmp}$
- (c)  $50\ \text{Amp}$
- (d)  $2\ \text{Amp}$

9. A system with an input power of 70 watts and an output power of 25 watts has an efficiency in percent of

a

b

- (a) 1%  
(b) 35.7%  
(c) 2.8%  
(d) 50%

c

d

10. How many joules of energy will a 15 watts lamp dissipates in one hr?

a

b

- (a) 54000 joules  
(b) 540 joules  
(c) 5400 joules  
(d) 54 joules

c

d

11. If a voltage in a circuit changes from 4 V to 8 V and the current in the same circuit changes from 3 mA to 5 mA, the resistance of the circuit is:

a

b

- (a) 5  $\Omega$   
(b) 1 k $\Omega$   
(c) 10  $\Omega$   
(d) 2 k $\Omega$

c

d

12. For the circuit shown in Fig 1, the equivalent resistor for this circuit is:

- (a) 3 k $\Omega$   
(b) 0  $\Omega$   
(c) 4.4 k $\Omega$   
(d) 2  $\Omega$

a

b

c

d

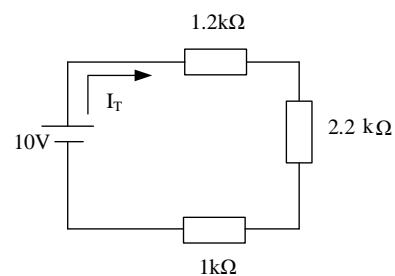


Fig 1

13. For the same circuit shown in Fig 1, the total current flowing from the battery equals to:

a

b

- (a) 5.1 mAmp  
(b) 2.27 mAmp  
(c) 10 mAmp  
(d) 2.5 mAmp

c

d

14. For the same circuit shown in Fig 1, the total power dissipated in the circuit equals to

(a) 11.5 mW  
 (b) 22.7 mW  
 (c) 2.1 mW  
 (d) 0 mW

a

b

c

d

15. For the circuit shown in Fig 2, the power dissipated by R5 is equal to:

(a) 4 mW  
 (b) 5 mW  
 (c) 10 mW  
 (d) 11 mW

a

b

c

d

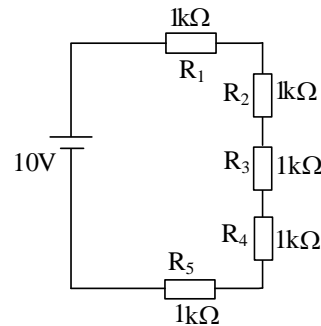


Fig 2

16. For the circuit shown in Fig 2, if R3 is short-circuited, how much power is dissipated in the circuit?

(a) 0.15 W  
 (b) 1 W  
 (c) 0.025 W  
 (d) 10 W

a

b

c

d

17. For the circuit shown in Fig 3, state which of the following KVL equations is correct:

(a)  $+10 + V_1 + V_2 - 15 + V_3 = 0$   
 (b)  $+10 - V_1 - V_2 - 15 - V_3 = 0$   
 (c)  $-10 - V_1 - V_2 + 15 - V_3 = 0$   
 (d)  $+10 - V_1 - V_2 + 15 - V_3 = 0$

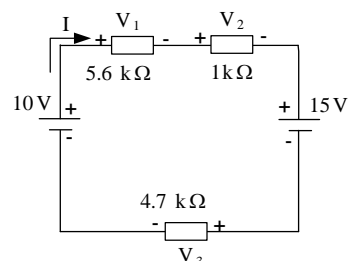


Fig 3

a

b

c

d

18. If the voltage drop across a resistor increases by a factor of 2 (double), the power dissipated by the resistor

(a) increases by a factor of 4  
 (b) increases by a factor of 200.  
 (c) increases by a factor of 10  
 (d) decreases.

a

b

c

d

19. For resistors in a series circuit, state which of the following statements is correct.

☐ a☐ b

- (a) Each resistor dissipates the same power, regardless of its resistance value.
- (b) Large-value resistors dissipate more power than small-value resistors,
- (c) Small-value resistors dissipate more power than large-value resistors
- (d) The smallest resistor drops the largest voltage

☐ c☐ d

20. Kirchhoff's current law states that:

☐ a

- (a) the sum of the currents around a closed loop is zero
- (b) the sum of the currents entering a junction must equal the sum of the currents leaving the junction
- (c) the sum of the currents entering a junction must equal zero
- (d) the total current entering a given junction is constant, even with changes in supply voltage.

☐ b☐ c☐ d

21. As shown in Fig 4, a  $6.8\text{ k}\Omega$  resistor and a  $2.2\text{ k}\Omega$  resistor are connected in parallel across a  $10\text{ V}$  battery. The total resistance of the circuit is:

- (a)  $2.7\text{ k}\Omega$
- (b)  $1.662\text{ k}\Omega$
- (c)  $9\text{ k}\Omega$
- (d)  $1\text{ k}\Omega$

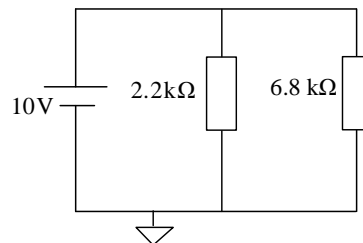


Fig 4

☐ a☐ b☐ c☐ d

22. For the circuit shown in Fig 4, the current flowing in the circuit is equal to:

- (a)  $3\text{ mA}$
- (b)  $1\text{ mA}$
- (c)  $4\text{ mA}$
- (d)  $6\text{ mA}$

☐ a☐ b☐ c☐ d

23. For the circuit shown in Fig 5, the total resistance  $R_T$  equals to:

(a)  $5.1 \text{ k}\Omega$   
(b)  $12.5 \text{ k}\Omega$   
(c)  $1.23 \text{ k}\Omega$   
(d)  $4.5 \text{ k}\Omega$

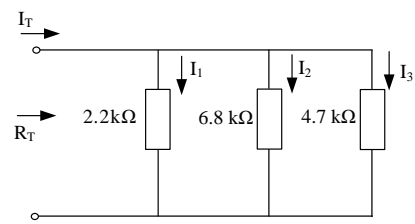


Fig 5


a  
b  
c  
d

24. For the circuit shown in Fig 5, if the total current  $I_T = 10 \text{ mA}$  then  $I_2$  equals to:

(a)  $1.5 \text{ mA}$   
(b)  $1.8 \text{ mA}$   
(c)  $1.0 \text{ mA}$   
(d)  $10 \text{ mA}$

a  
b  
c  
d

25. For the circuit shown in Fig 6:

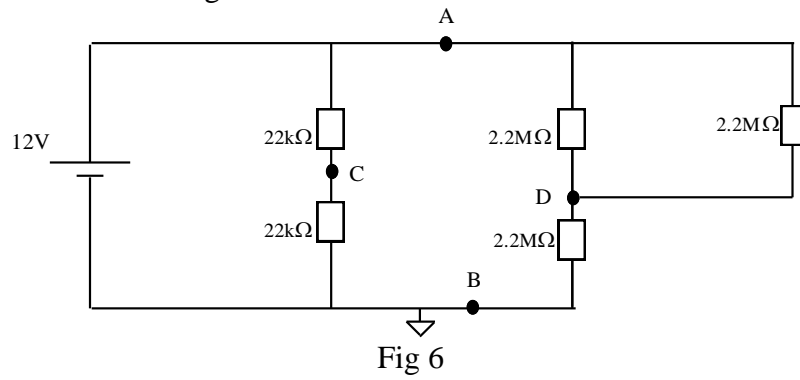

Complete Table 1 (show all calculation)

**Table 1**

$V_{AB} =$	$V_{AD} =$
	$V_{DB} =$
	$V_{CB} =$

26. For the circuit shown in Fig 7:

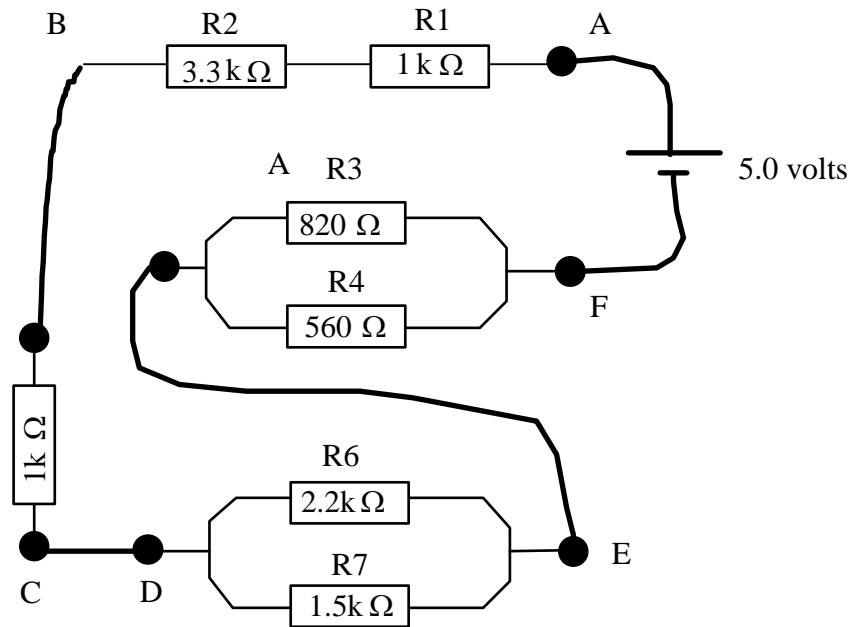


Fig 7

a. Calculate the equivalent resistance of the circuit. (Show all work).

b. Calculate the total current in the circuit.



27. For the circuit shown in Fig 8:

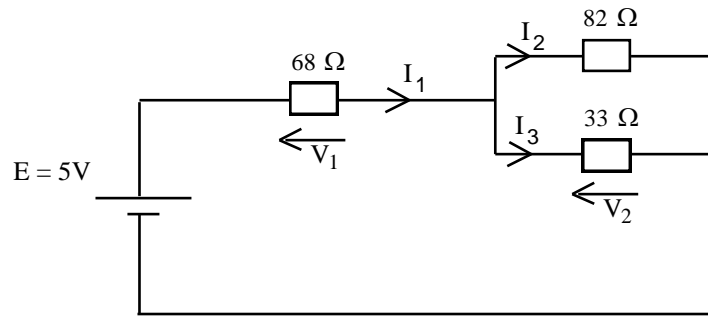


Fig 8

a. Calculate currents  $I_1$ ,  $I_2$ ,  $I_3$  and voltages  $V_1$  &  $V_2$